



# Mid-Atlantic Antique Radio Club

*Collecting and Preserving Our Electronics Heritage*


## **METER REPLACEMENT**

Dave Rossetti  
16 December 2018


---
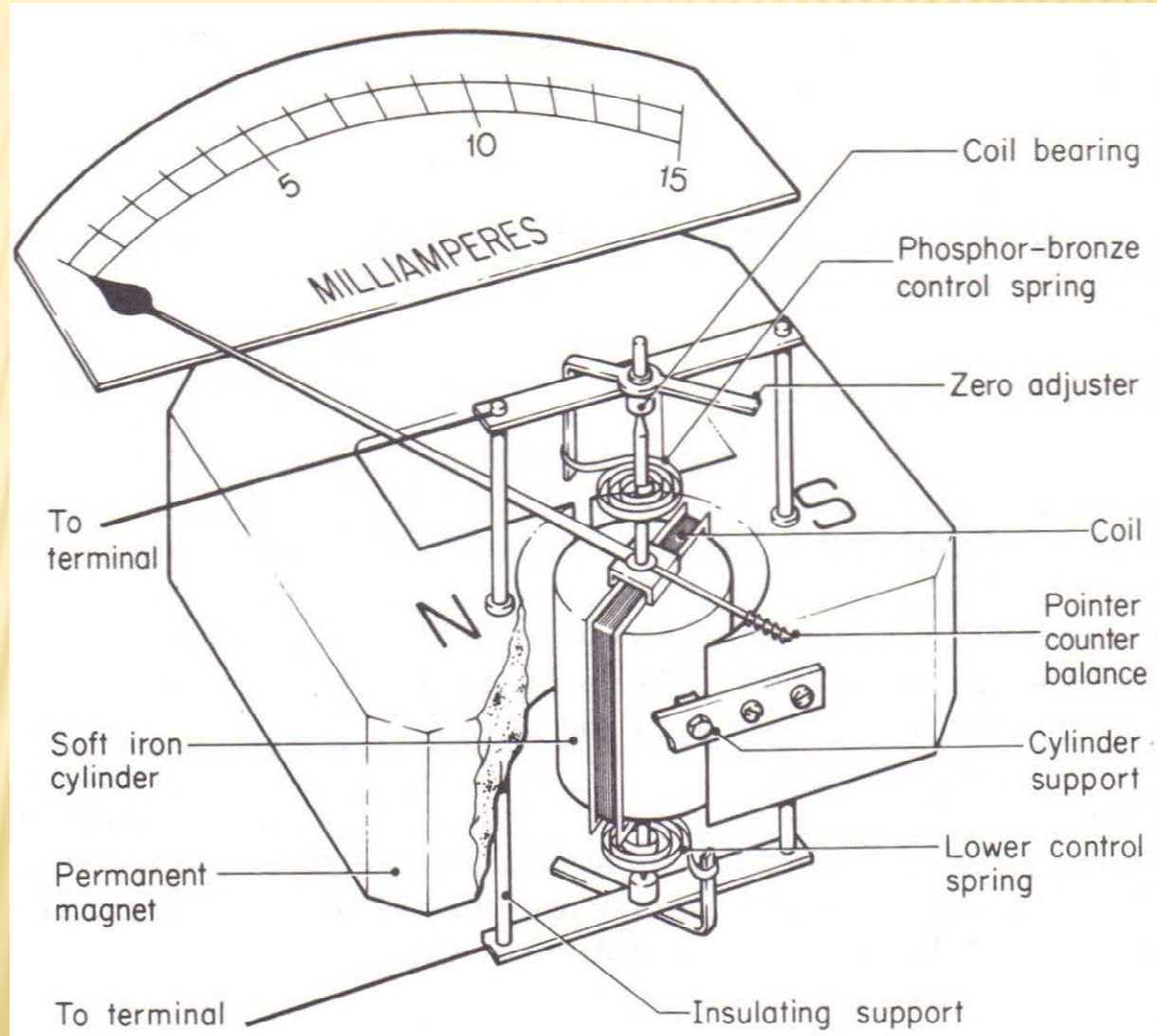
# METER CONSTRUCTION – D'ARSONVAL MOVEMENT

- Permanent magnet
- Soft iron cylinder and coil
- Control springs
- Zero adjuster
- Coil bearings
- Pointer counter balance
- Terminal feeds



# ONE METER – MULTIPLE APPLICATIONS

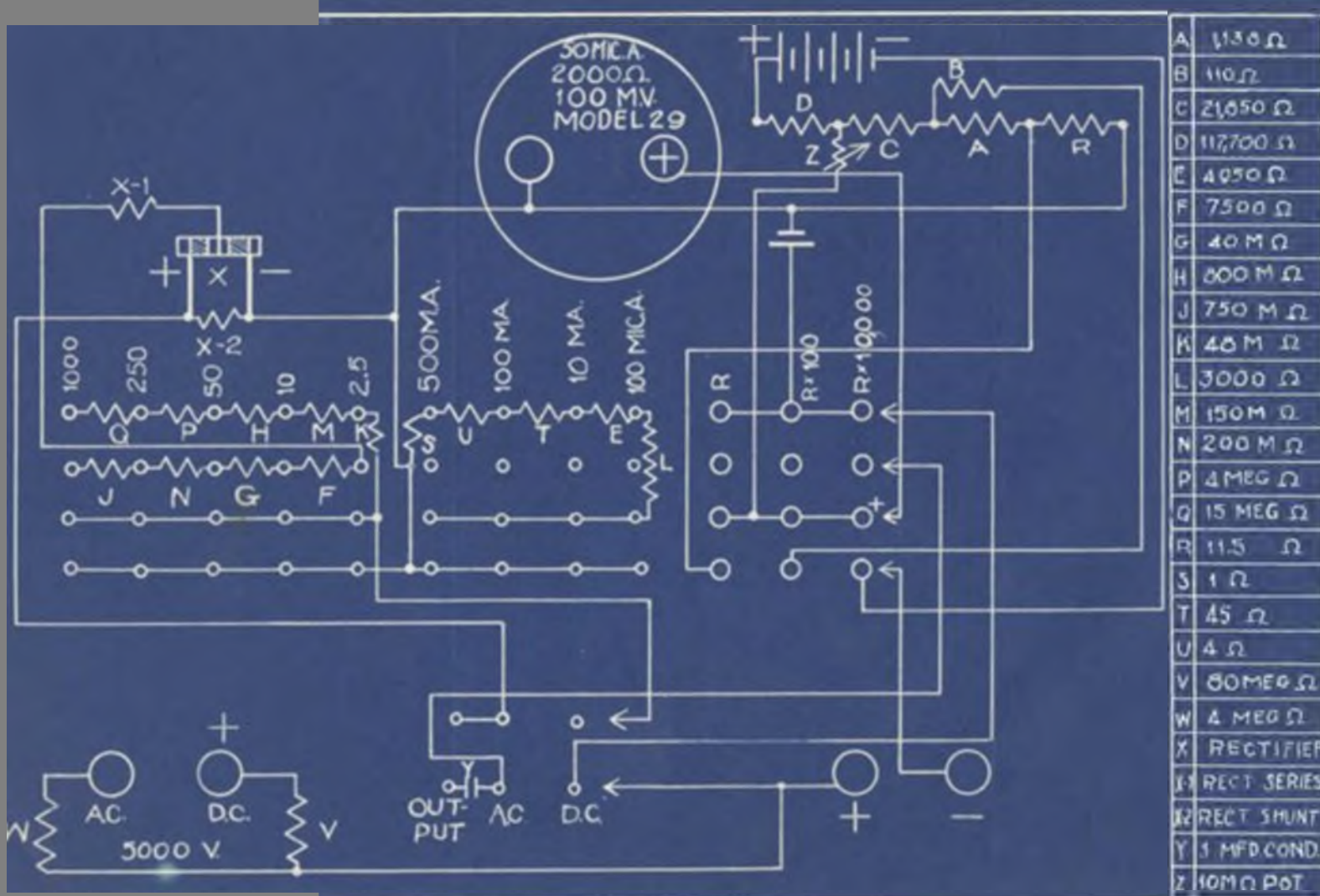

A	1130 Ω
B	110 Ω
C	21,050 Ω
D	117,700 Ω
E	4050 Ω
F	7500 Ω
G	40 M Ω
H	800 M Ω
J	750 M Ω
K	40 M Ω
L	3000 Ω
M	150 M Ω
N	200 M Ω
P	4 MEG Ω
Q	15 MEG Ω
R	11.5 Ω
S	1 Ω
T	45 Ω
U	4 Ω
V	80 MEG Ω
W	4 MEG Ω
X	RECTIFIER
Y	RECT SERIES
Z	RECT SHUNT
Y	1 MFD COND.
Z	10M Ω POT.


# METER CHARACTERISTICS

---

- Most meters are very linear
- Full Scale (f.s.) Sensitivity
  - Generally in milliamperes (mA) or microamperes ( $\mu\text{A}$ ) (higher values achieved using shunt resistors)
  - Determined by the number of windings - the more windings, the greater the magnetic field generated, and the more sensitive the meter
- Internal Resistance
  - ohms ( $\Omega$ )
  - Also determined by the number of windings - the more windings, the greater the internal resistance
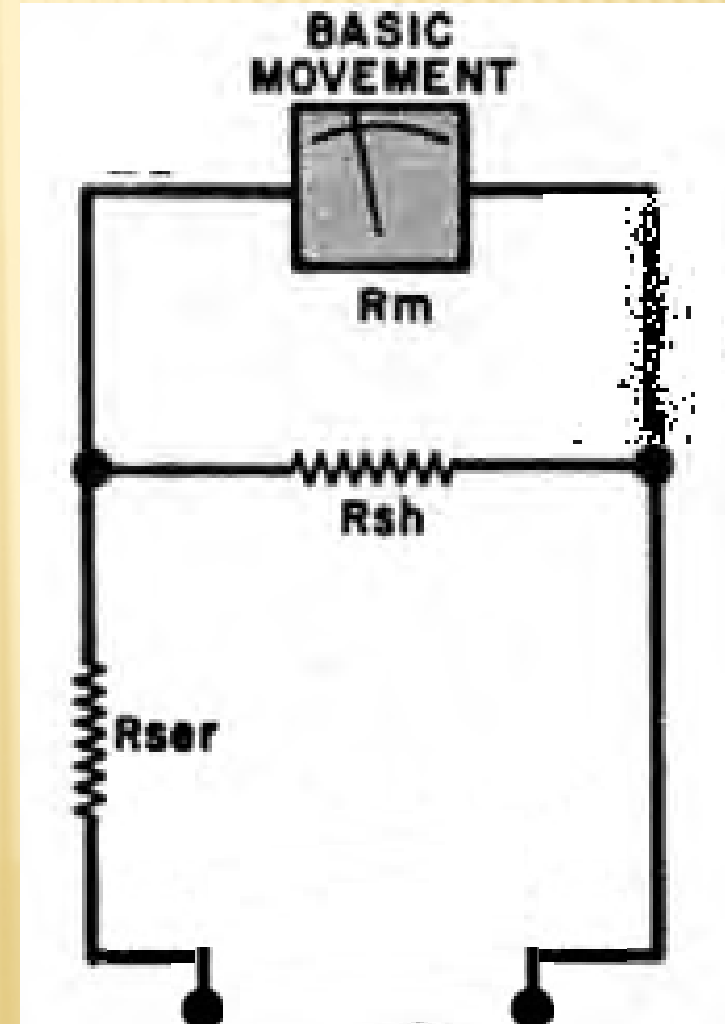
# METER 'TRIMMING'


- Many meters use a resistor in series ( $R_{ser}$ ) to bring the meter up to the desired Internal Resistance ( $R_m$ )
- Meters can also have a shunt ( $R_{sh}$ ) to adjust their f.s. sensitivity
- Resistors may be internal or external to the meter


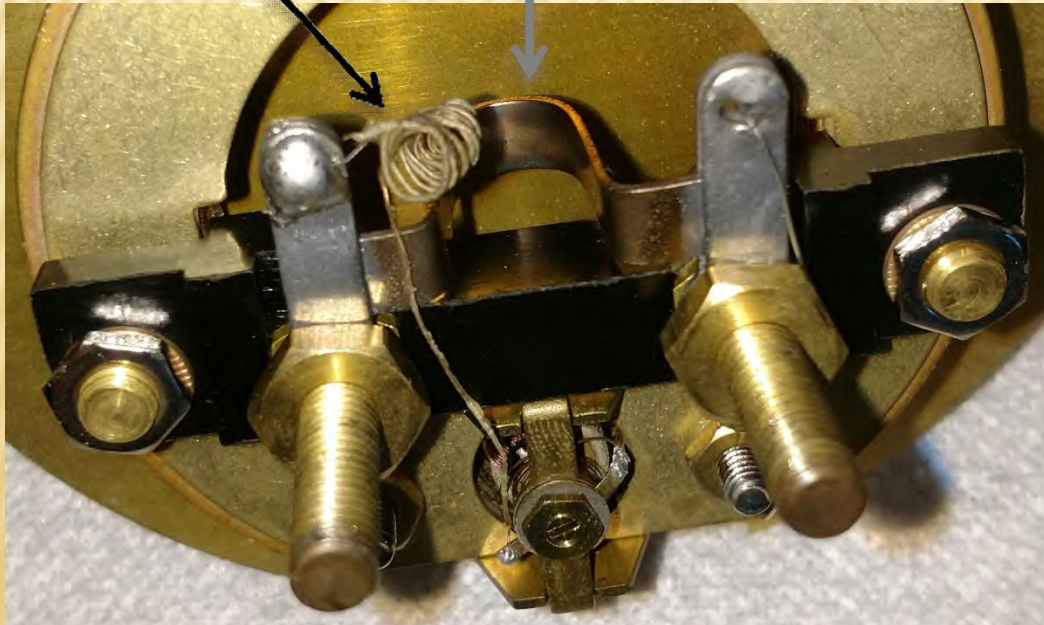
# METER RESISTOR EXAMPLES

In series wire coil resistor to bring meter up to internal resistance

In parallel shunt resistor to reduce total meter f.s. sensitivity (10 A meter, low resistance shunt)





In parallel wire spool shunt resistor to reduce total meter f.s. sensitivity

# METER USES

- D'Arsonval meters measure D.C. amperage (current) when positioned in series to the load
  - Shunt resistors (in parallel to the meter) allow the same meter to have lower sensitivity and measure higher amperages
- D'Arsonval meters positioned in parallel to the load measure D.C. voltage
  - Resistors in series to the meter (multipliers) allow the same meter to measure higher voltages
- D'Arsonval meters can also be used as an ohmmeter
- D'Arsonval meters used in conjunction with a diode bridge will measure A.C.
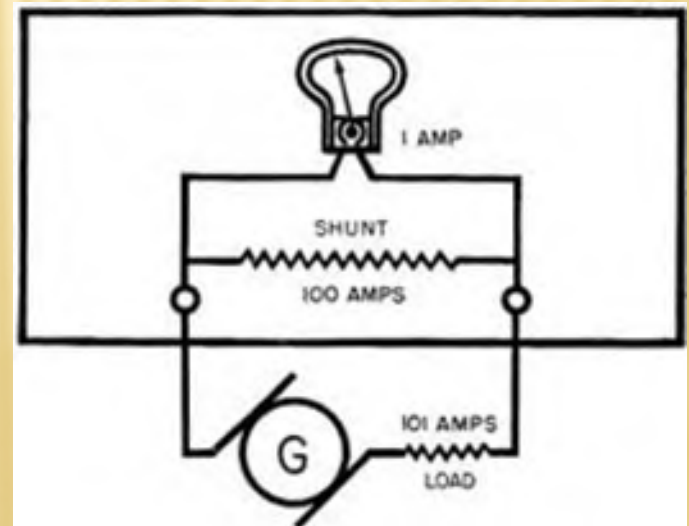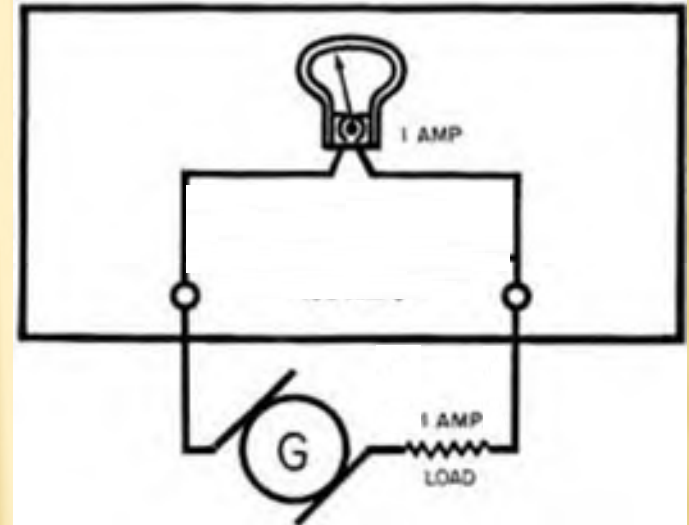
# AMMETER


- A 1 amp ammeter measures up to a 1 amp load as (as produced by generator [G])
- Add a 100 amp shunt resistor and a 1 amp ammeter can measure up to a 101 amp load






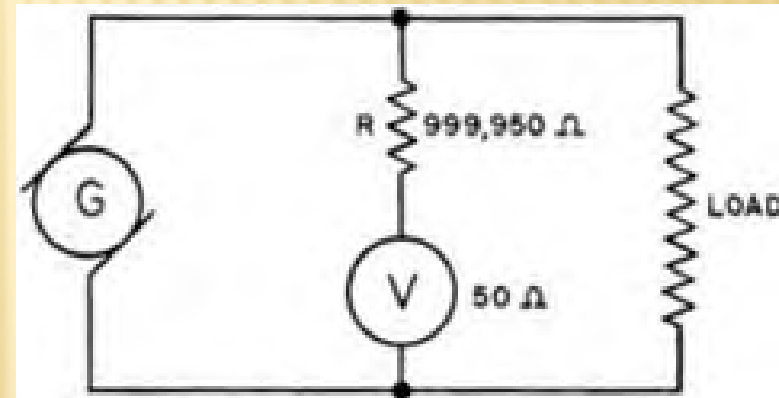
# VOLTMETER

- The same voltage potential (from generator [G]) exists across the load and across the meter and multiplier resistor (R)
- If voltmeter has  $50\Omega$  internal resistance, and a f.s. sensitivity of  $500\text{ mA}$  ( $.0005\text{ A}$ ), and you add a  $999,950\Omega$  resistor in series with the meter, it presents a  $1\text{M}\Omega$  resistance across the voltage potential
- This  $500\text{mA}$  ammeter will measure:  
 $V = IR = .0005\text{A} \times 1,000,000\Omega = 500\text{V}$  f.s. as a voltmeter
- Reduce voltage to  $250\text{V}$ , meter will read half scale



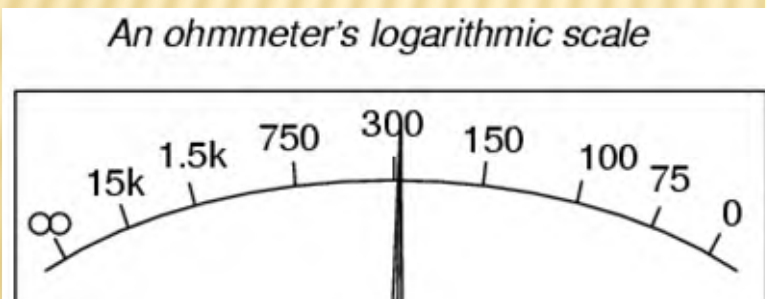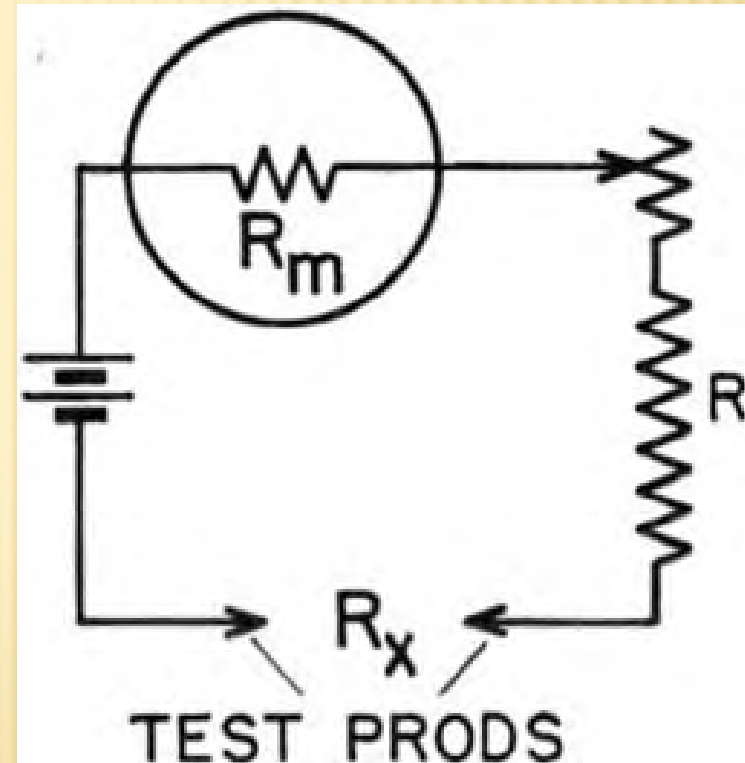
# OHMMETER

- Resistor ( $R$ ) and the meter resistance ( $R_m$ ) are in series with a D.C. voltage source and a variable resistor
- When test prods are shorted ( $0\Omega$ s), the variable resistor is adjusted to cause the meter to read full scale – f.s. =  $0\Omega$ s
- Increased resistance across the test prods decreases circuit current and causes the meter to read less than f.s.
- Meter scale is calibrated to read resistance in ohms



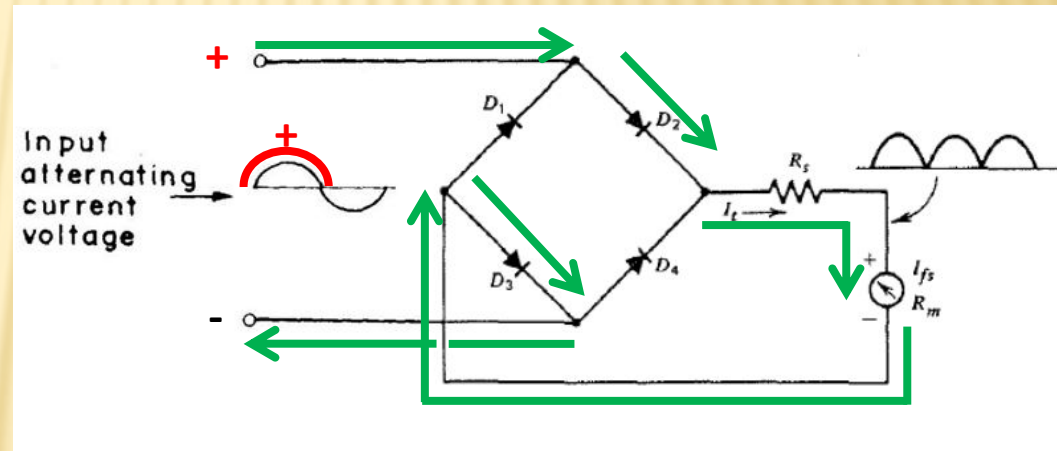
# A.C. VOLTMETER

- D'arsonval meter measures D.C. amperage
- When A.C. voltage is positive at the top lead and negative at the bottom lead, current flows through Diode  $D_2$ , through the in series multiplier resistor ( $R_s$ ), through the meter, through diode  $D_3$ , and to the bottom lead



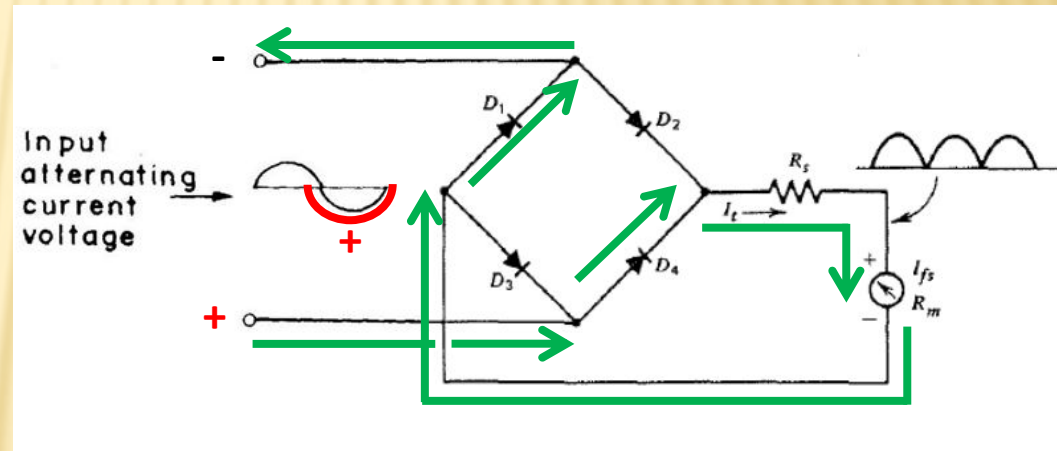
# A.C. VOLTMETER

- When A.C. voltage is positive at the bottom lead and negative at the top lead, current flows through Diode  $D_4$ , through the in series multiplier resistor ( $R_s$ ), through the meter, through diode  $D_1$ , and to the top lead


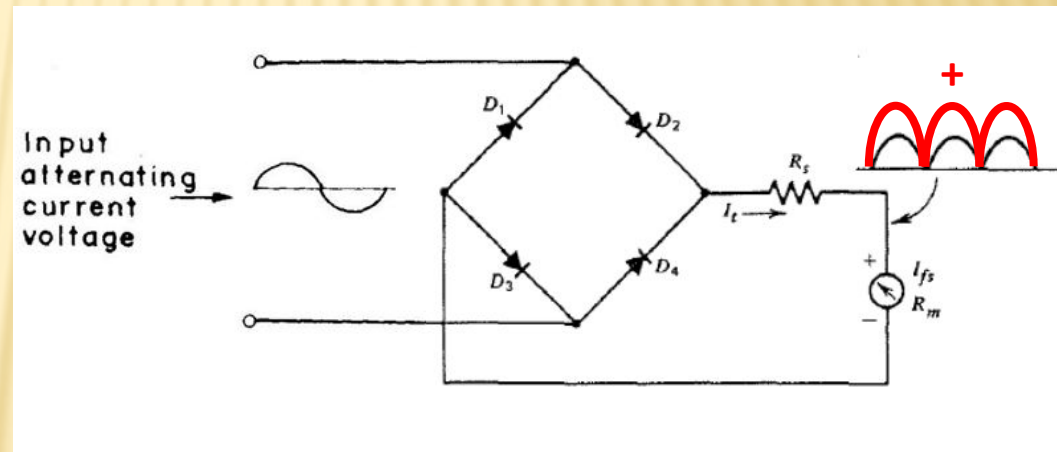
# A.C. VOLTMETER

- The meter reads the root mean square (RMS) of the voltage



# METER ISSUES

- Sticky meter – Pointer stops at some point on the scale
  - Usually caused by lint, dirt, or metal chips touching the coil or pointer
  - Remove debris with a small sharp object or masking tape
  - Do not touch the delicate springs or coil
- Friction – slow movement, and when tapped, point moves
  - Usually caused by dirty or dull pivots, or cracked bearings
  - May be able to loosen the jewel screw, or may not be repairable
- Balance – Meter zeros differently when horizontal or vertical
  - Usually caused by poorly adjusted pointer counter balance
  - Pointer may have adjustable weights, a flexible "tail weight" which is bent until balanced, or adding weight using quick-drying paint or shellac
- Static charge affecting meter movement
  - Use an antistatic spray, or make your own (8oz water, 2 oz rubbing alcohol, and a drop or two of dishwashing liquid soap)
- Check for loose internal resistors – re-solder
- Burnt springs or coils are not repairable – must replace the meter

# METER REPLACEMENT

---

- “Any moving-coil meter can be replaced with another of the same or greater sensitivity” – Alan Douglas
- Most meter movements can be refurbished and custom designed to suit just about any metering need imaginable
- The process is relatively simple



# DETERMINING A SUITABLE REPLACEMENT METER

- The replacement meter must have:
  - the same or less f.s. sensitivity (in amps, mA, or  $\mu\text{A}$ )
  - the same or less equivalent f.s. voltage determined by multiplying the f.s. amperage by the internal resistance in ohms (generally in mV)
- Schematics usually show the required meter sensitivity and internal resistance
- Will want the meter to have the same characteristics as the original meter
  - Same shape (round, rectangular, square)
  - Same size
  - Same style (glass lens, plastic lens, classic look, modern look)
  - Same movement arc (typically 90 degrees)


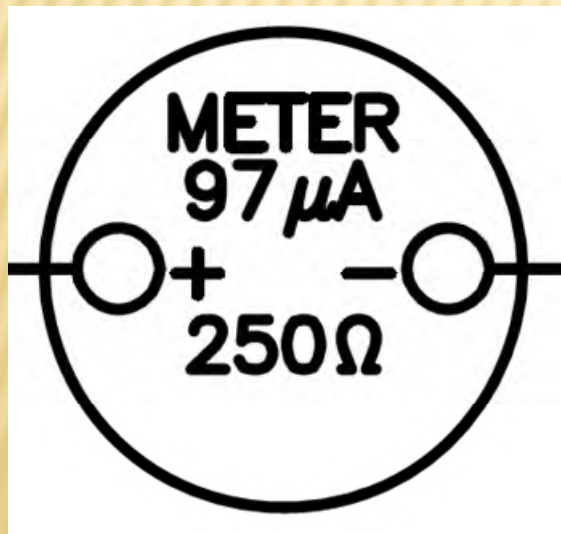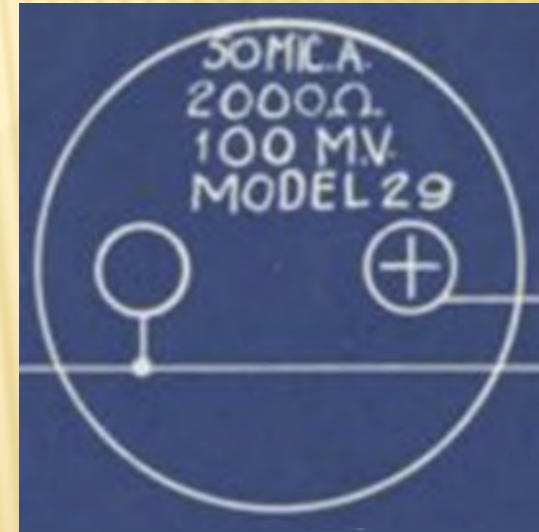
# STEP 1 - DETERMINING REQUIRED METER SENSITIVITY


- Most schematics show meter characteristics
- Simpson Multimeter - 50 mA f.s.  
2,000 $\Omega$  internal resistance,  
100 mV f.s. = 50mA x 2,000 $\Omega$



- Hickok 539A  
97 $\mu$ A f.s.  
250 $\Omega$  internal resistance,  
24.25 mV f.s. = 97 $\mu$ A x 250 $\Omega$

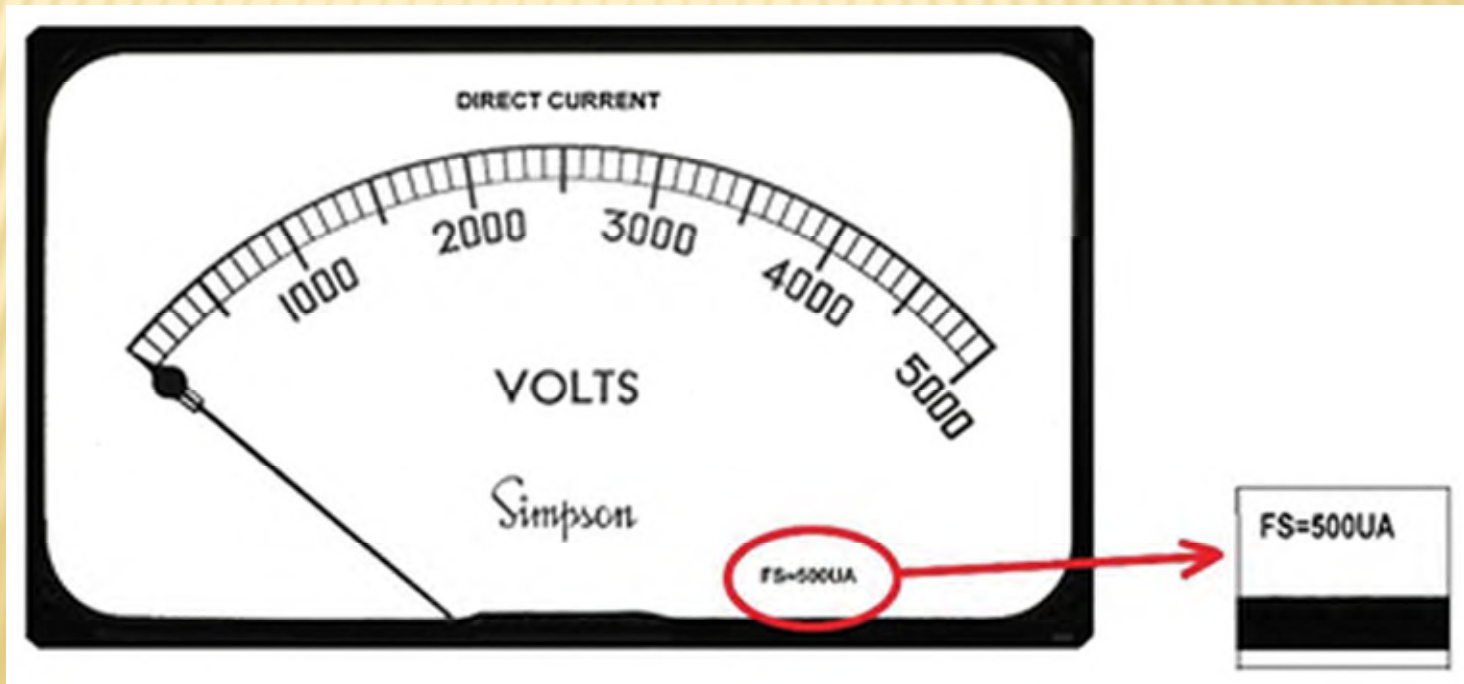
# STEP 2 - DETERMINING METER SENSITIVITY

- Some meters show f.s. current on the meter face
- f.s.=500 $\mu$ A - indicating need for a 10 M $\Omega$  series multiplier resistor
- Best to measure to ensure it is in spec


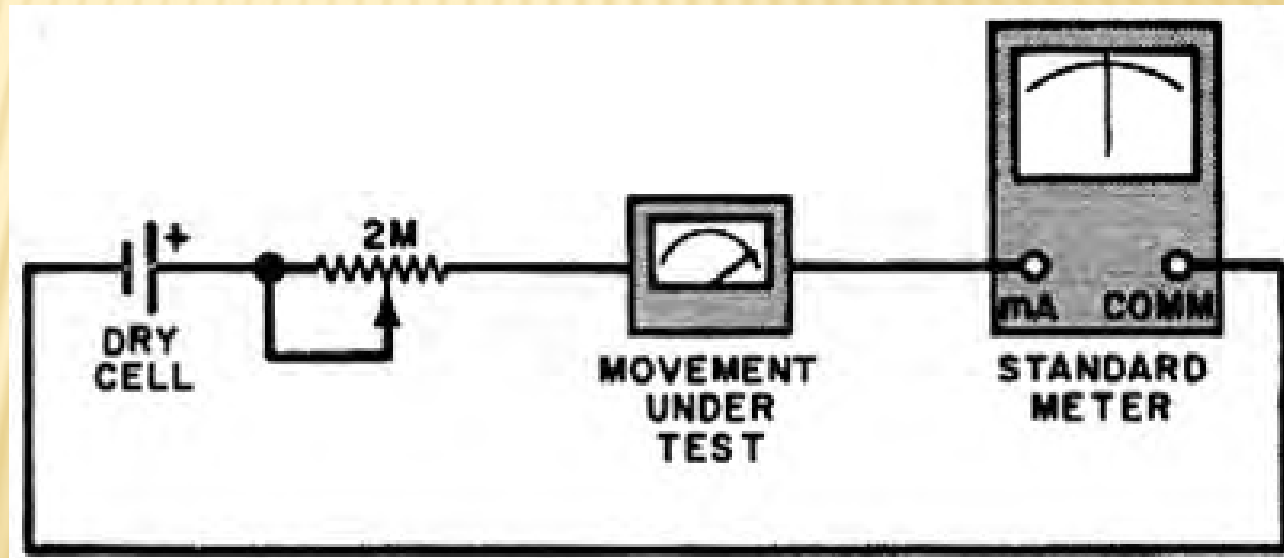
# STEP 2A - DETERMINING METER SENSITIVITY

- Using a 1.5V battery, a 1MΩ or 2MΩ pot, and an ammeter, measure the f.s. sensitivity
- Turn pot to max before connecting the battery
- Adjust until the meter under test swings to full scale
- Both meters in series read the same current
- Measure the f.s. amperage



# STEP 2A - DETERMINING METER SENSITIVITY



# STEP 3 – DETERMINE INTERNAL RESISTANCE

- WARNING – The current supplied by an ohmmeter can damage the movement
- NEVER USE AN ANALOG VOLT METER TO MEASURE INTERNAL RESISTANCE
  - A Simpson 260 can supply 100mA into a low resistance
- Unless you know the meter internal resistance is  $> 1\text{mA}$ , DO NOT USE A DIGITAL OHMMETER TO MEASURE INTERNAL RESISTANCE
  - Even a self-ranging digital ohmmeter can exceed the meter f.s. limit


# STEP 3 – DETERMINE INTERNAL RESISTANCE

## – USING A VOLTMETER

- A simple method of measuring internal resistance is to measure the current at full scale deflection with a digital ammeter (DMM1), and the voltage drop across the meter (equivalent f.s. voltage) with a digital voltmeter (DMM2)

- Apply Ohms Law:

- $R = V(\text{f.s.}) / I(\text{f.s.})$

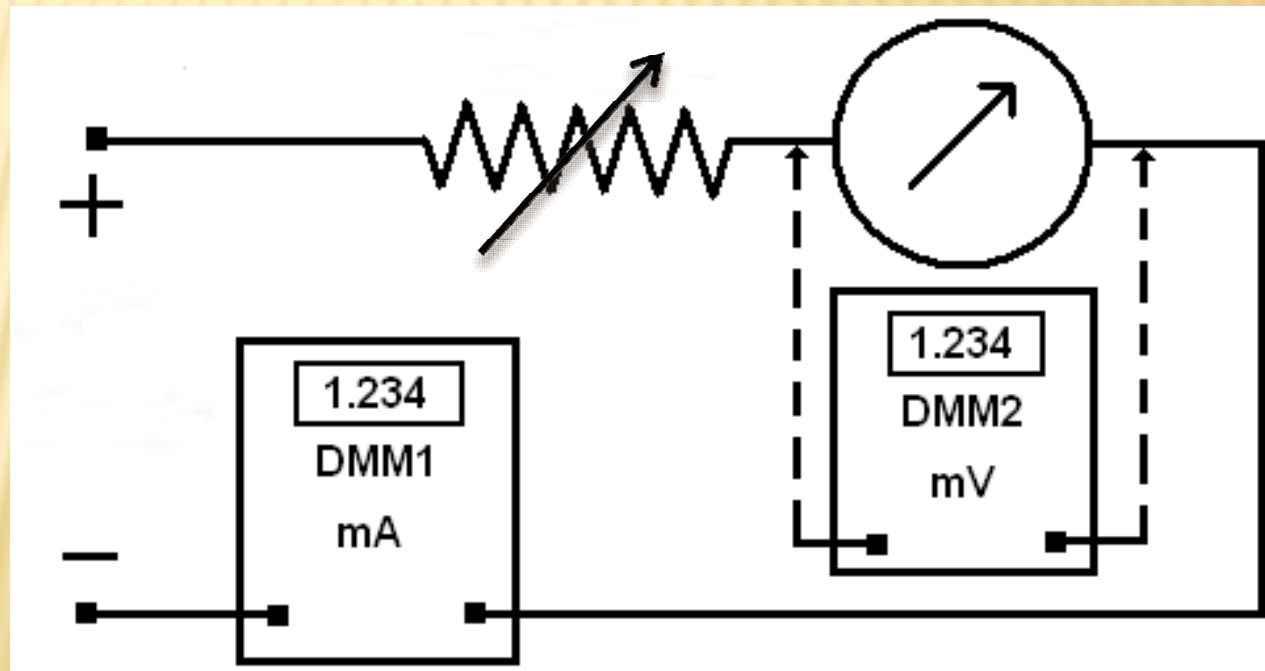


# STEP 3 – DETERMINE INTERNAL RESISTANCE – USING A VOLTMETER

- $R = V(\text{f.s.}) / I(\text{f.s.})$
- $R = 68\text{mV} / 50\mu\text{A}$
- $R = .068 \text{ V} / .00005\text{A}$
- $R = 1,360 \Omega$



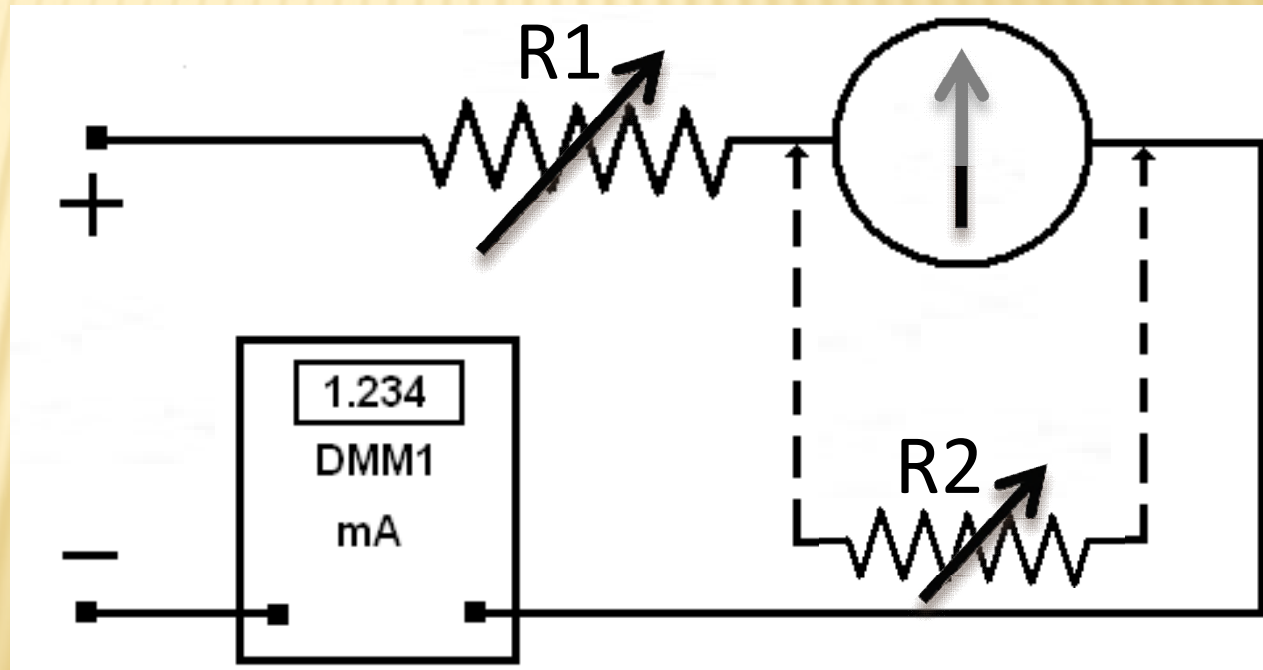
# STEP 3A – DETERMINE INTERNAL RESISTANCE – USING A RESISTOR

- Another method of measuring internal resistance is to place a resistor decade box or a variable resistor across meter ( $R_2$ )
- Increase the resistance of  $R_2$  until the meter reads half scale.
- Tweak  $R_1$  and  $R_2$  so that the digital ammeter (DMM1) reads exactly full scale current, and the meter under test reads exactly half scale
- $R_2$  equals the meter internal resistance





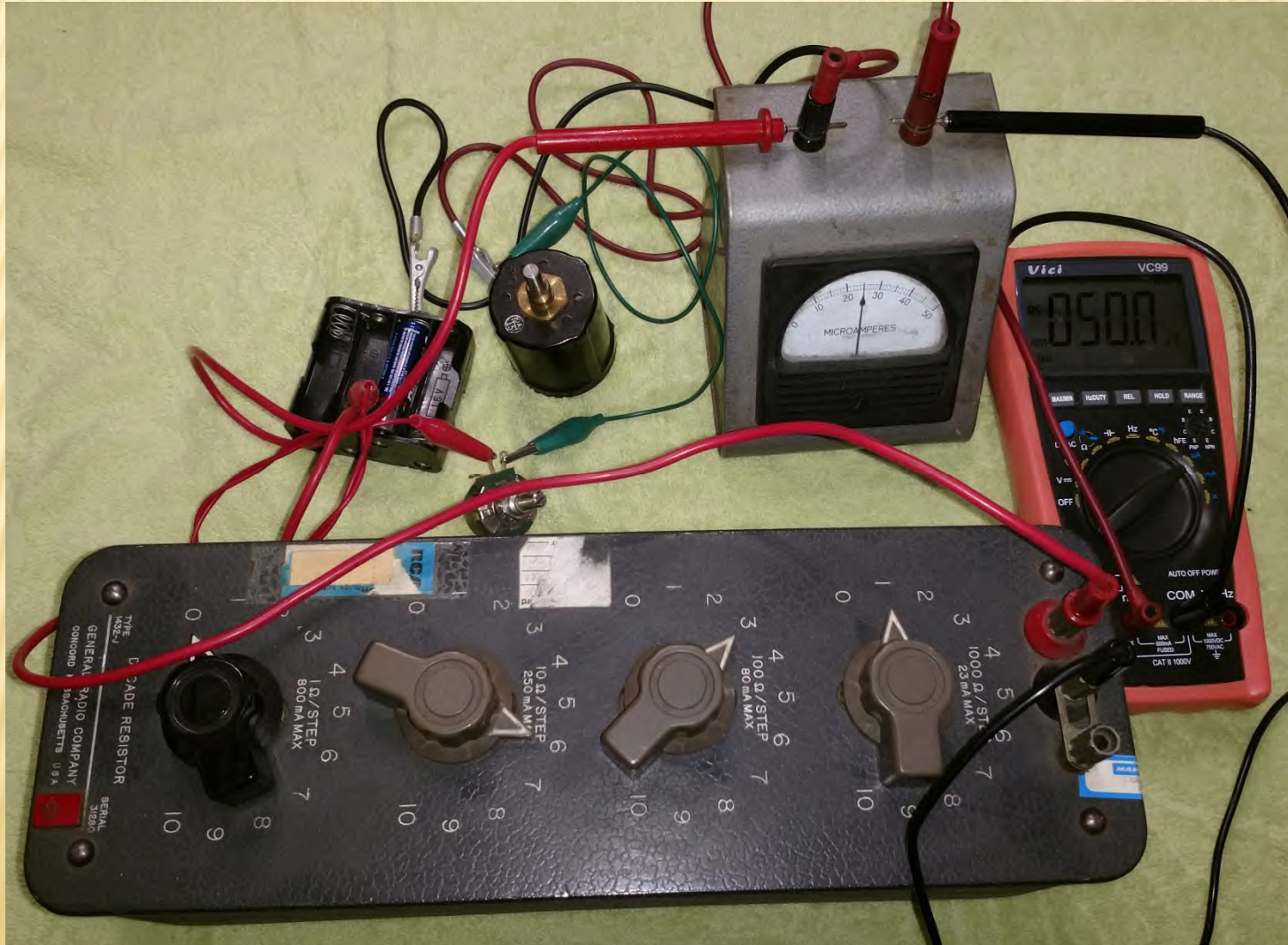
# STEP 3A – DETERMINE INTERNAL RESISTANCE – USING A RESISTOR (1,360Ω)



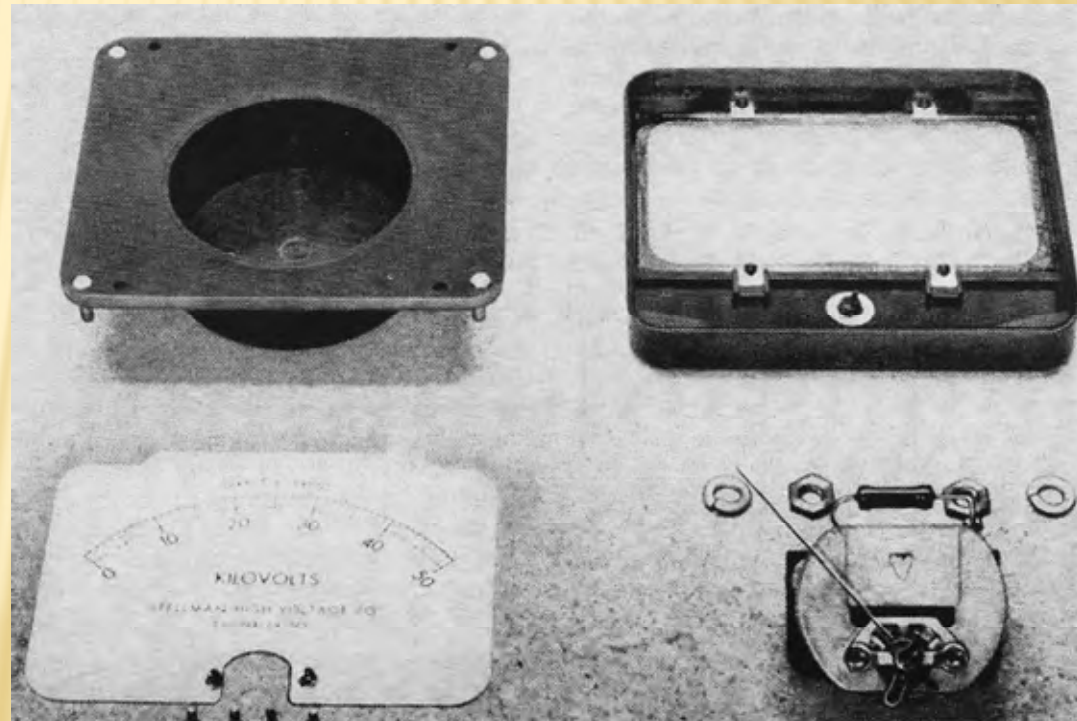
# STEP 4 - CLEAN AND DISASSEMBLE CANDIDATE METER

- Clean away all foreign material from case
- Use warm water and soap (rubbing alcohol for greasy buildups)
- Internal resistors may be retained or disposed of (depending on desired use)


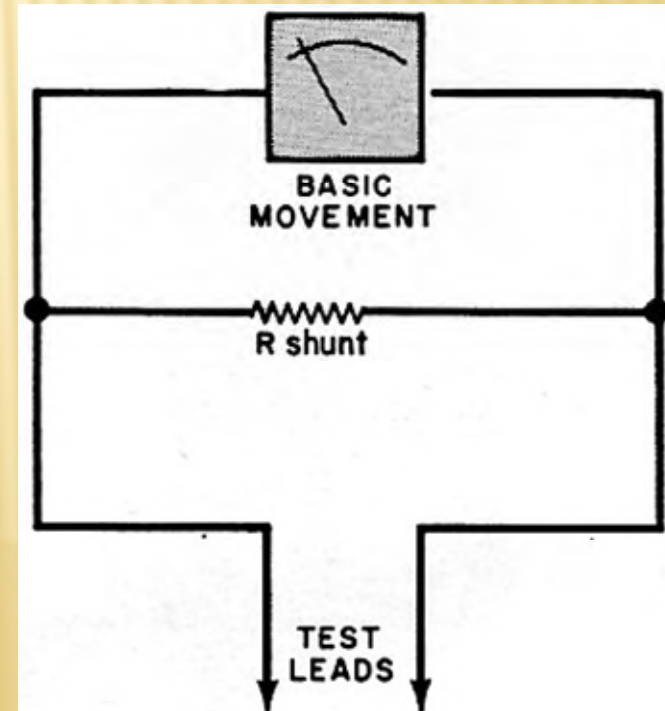
# STEP 6 – DETERMINE SHUNT VALUE

- Knowing the Internal Resistance (IR) of the candidate meter ( $R_m$ ), and its f.s. current ( $I_m$ ), we can calculate the shunt required to bring the meter to the correct sensitivity
- $R_{shunt} = R_m \times I_m / I_{max} - I_m$
- To shunt a  $50\mu A$  meter to handle a  $100\mu A$  current, and the candidate meter has an internal resistance of  $1,360\Omega$
- $$\begin{aligned} R_{shunt} &= 1,360\Omega \times 50\mu A / 100\mu A - 50\mu A \\ &= 1,360 \times .00005 / .0001 - .00005 \\ &= 1,360 \times .00005 / .00005 \\ &= 1,360 \Omega \end{aligned}$$
- To shunt a  $50\mu A$  meter to handle a  $200\mu A$  current, with the same candidate (internal resistance of  $1,360\Omega$ )
- $$\begin{aligned} R_{shunt} &= 1,360\Omega \times 50\mu A / 200\mu A - 50\mu A \\ &= 1,360 \times .00005 / .0002 - .00005 \\ &= 1,360 \times .00005 / .00015 \\ &= 453.33 \Omega \end{aligned}$$



# STEP 7 – DETERMINE SERIES VALUE TO BRING SUBSTITUTE METER TO SAME IR

- Knowing the Internal Resistance (IR) of the candidate meter ( $R_m$ ), and the shunt value required to bring the meter to the correct sensitivity ( $R_{shunt}$ ), we can determine the total resistance of the shunted meter ( $R_t$ )
- $R_t = R_m \times R_{shunt} / R_m + R_{shunt}$
- A  $50\mu A$  meter with a  $1,360\Omega$  internal resistor, shunted with a  $1,360\Omega$  shunt  
 $R_t = 1,360 \times 1,360 / 1,360 + 1,360 = 680 \Omega$
- If the original meter had a resistance of  $700 \Omega$ , we add a  $20 \Omega$  resistor to bring it to spec ( $680 \Omega + 20 \Omega = 700 \Omega$ )
- A  $50\mu A$  meter with a  $1,360\Omega$  internal resistor, shunted with a  $453.33\Omega$  shunt  
 $R_t = 1,360 \times 453.33 / 1,360 + 453.33 = 340 \Omega$
- If the original meter had a resistance of  $400 \Omega$ , we add a  $60 \Omega$  resistor to bring it to spec ( $340 \Omega + 60 \Omega = 400 \Omega$ )


# CREATING PRECISION RESISTORS

---

- Calculated value for needed resistor will not be readily available
- Arrange two or more resistors in series/parallel hookups to yield the required value

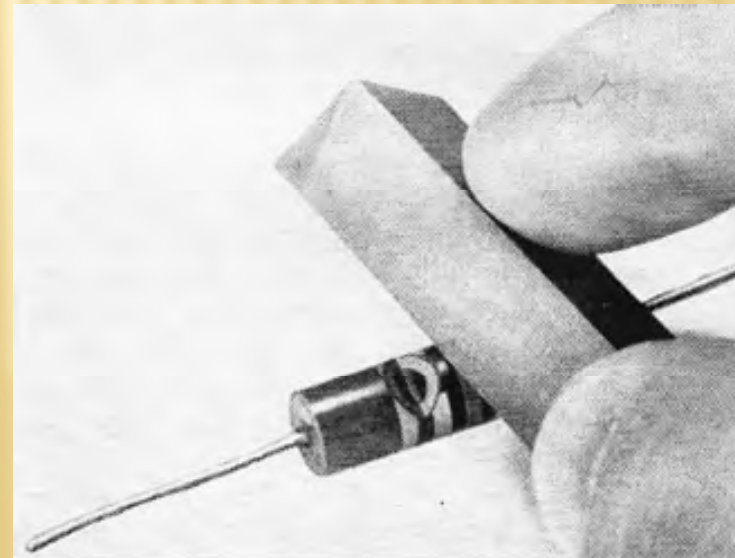
# CREATING PRECISION RESISTORS

- Alternatively, "trim" an ordinary carbon resistor with a file
- Select a fixed resistor of slightly lower value than required
- Use a resistance bridge or an ohmmeter to monitor your progress
- Once trimmed to the proper value, coat the notch with coil dope or nail polish to seal out moisture


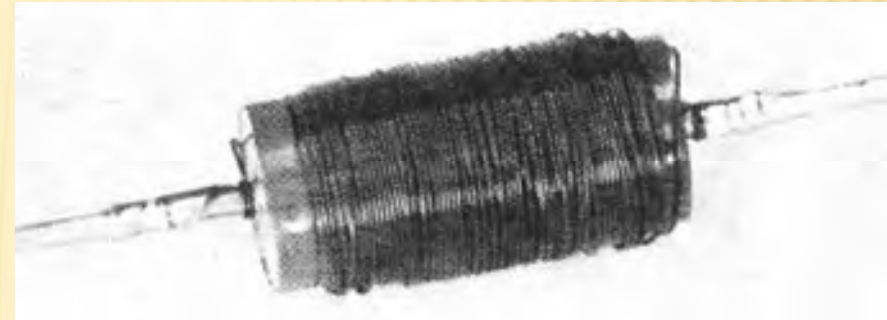
# CREATING PRECISION RESISTORS

- For very low value resistors, wind your own
- Use enamel-coated copper wire wrapped around a high-value resistor (1 M $\Omega$  will do)
- Wire gauges and the resistance they yield are given in the Table
- After winding solder the wire's ends to the resistor leads
- Coat the assembly with coil dope or nail polish



<b>Gauge</b>	<b>Ohms per 1000 ft.</b>	<b>Gauge</b>	<b>Ohms per 1000 ft.</b>
18	6.510	30	105.2
20	10.35	32	167.3
22	16.46	34	266.0
24	26.17	36	423.0
26	41.62	38	672.6
28	66.17	40	1069.0

# STEP 8 – RELABEL THE NEW METER

---

- Can scan the original meter scale
  - Resize if necessary
  - Print on Card Stock or on vinyl media using either Inkjet or Laser printer
    - <https://www.papilio.com/>
    - <https://duradecal.com/>
- Create a new meter scale
  - Tonne Software Meter
    - <http://www.tonnesoftware.com/>



# METER REPLACEMENT EXAMPLE

- Original Equipment Meter – Hickok 539A
  - 97 $\mu$ A f.s. sensitivity
  - 250 $\Omega$  Internal Resistance
- Meter must have f.s. sensitivity < 97 $\mu$ A
- Meter must have equivalent f.s. voltage less than that calculated using  $V=IR$
- $V=97\mu\text{A} \times 250\Omega = .000097\text{A} \times 250\Omega = .02425 \text{ V}$  or 24.25 mV
- Meter must have equivalent f.s.  $V < 24.25 \text{ mV}$

# HICKOK TUBE TESTER METERS (PARTIAL LIST)

Ohm's Law  
 $V=IR$

Model	Sensitivity f.s.	Internal Resistance, ohms	Equivalent mV f.s.
I-177	1.4 mA	80	112
560 (KS 9237)	1.4mA	80	112
533A	500 $\mu$ A	233	116
TV-3	200 $\mu$ A	2365	473
<i>(with VOM 1k ohms per volt)</i>			
TV-3C	50 $\mu$ A	1150	57.5
<i>(with VOM 20k ohms per volt)</i>			
TV-10D	200 $\mu$ A	2350	470
KS 15560	200 $\mu$ A	2365	473
KS 15750	120 $\mu$ A	1500	180
539C	115 $\mu$ A	1500	172.5
750	280 $\mu$ A	645	181
799	500 $\mu$ A		
6000A	100 $\mu$ A	1165	116.5
600	500 $\mu$ A		
605	50 $\mu$ A		
<i>(with VOM 20k ohms per volt)</i>			
TV-7	200 $\mu$ A	2355	471

# POSSIBLE CANDIDATES


	O.E.	50 $\mu$ A Candidate	Simpson 50 $\mu$ A	50 $\mu$ A Meter from earlier
Sensitivity (f.s.)	97 $\mu$ A	50 $\mu$ A	50 $\mu$ A	50 $\mu$ A
Internal Resistance (R=V/R)	250 $\Omega$	$\leq 485\Omega$	1,800 $\Omega$	1,360 $\Omega$
Equivalent f.s. Voltage (V=IR)	V=IR .02425 V or 24.25 mV	$\leq 24.25\text{mV}$	90mV	68mV
Comment			Not a viable candidate	Not a viable candidate

# REFERENCES

- ***Tube Testers and Classic Electronic Test Gear*** – Alan Douglas, 2000
- ***How to Make Custom Meters from Salvaged Parts, April 1974 Popular Electronics*** - Prof. Robert Koval
- ***Analog meters - The joy of movement*** - David Ashton - April 12, 2015 - <https://www.embedded.com/electronics-blogs/embedded-down-under/4439175/Analog-meters---The-joy-of-movement>
- ***Analog meters - Getting the most out of your meter*** - David Ashton - APRIL 29, 2015 - <https://www.embedded.com/electronics-blogs/embedded-down-under/4439317/Analog-meters---Getting-the-most-out-of-your-meter->
- ***Electricity - Basic Navy Training Courses, NAVPERS 10622*** – 1945 - Chapter 18 ELECTRICAL METERS
- ***Tonne Software*** - <http://www.tonnesoftware.com/>
- ***Papilo Vinyl Print Media*** - <https://www.papilio.com/>  
<https://duradecal.com/>
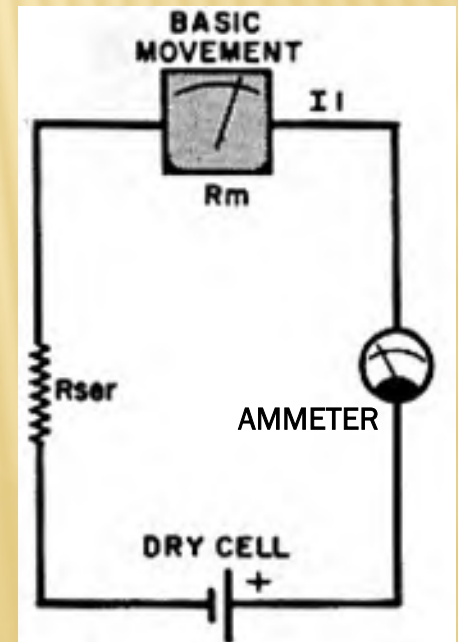
# STEP 3 – DETERMINE INTERNAL RESISTANCE

- To determine the meter's Internal Resistance ( $R_m$ ), use two resistors of known value, a 1.5V battery, an ammeter, and this circuit
- Chose a series resistor ( $R_{ser}$ ) using ohms law ( $V=IR$ ) to result in a current ( $I_1$ ) that will cause the meter under test to read in the top third of the meter scale
- Record the current ( $I_1$ ) on the ammeter



# STEP 3 – DETERMINE INTERNAL RESISTANCE

- Add a shunt resistor ( $R_{sh}$ ) that is  $1/10$  to  $1/20$  the value of the series resistor to the circuit and record the current ( $I_2$ )
- Knowing the resistor and current values, calculate the meter Internal Resistance ( $R_m$ ) using this formula:

$$R_m = \frac{R_{ser} \times R_{sh} \times (I_1 - I_2)}{R_{ser} \times I_2 + R_{sh} \times (I_2 - I_1)}$$

